 


M-3-3-B1: Design and implement the following using, (i) [logisim](#) (do not use inbuilt adder, subtractor, mux, dmux, etc. other than logic gates) (ii) [Verilog](#) (gate modelling, dataflow modelling and behavioral modelling) (**Note:** File naming should be done as, 16CO226-L3.circ (for logisim), 16CO226-VG3.v (for gate modelling), 16CO226-VD3.v (for dataflow modelling), 16CO226-VB3.v (for behavioral modelling), 16CO226-V3.v (input/data file along-with \$monitor for input and output) and 16CO226-V3.vcd (for waveform))

- (i) Convert JK to SR flip-flop
- (ii) Master Slave flip-flop using NAND gates
- (iii) D flip-flop with AND and NOR gates
- (iv) Given the state diagram draw its corresponding circuit diagram



Q. No.	Reg. No.
(i)	16CO101 - 16CO112
(ii)	16CO113 - 16CO123
(iii)	16CO124 - 16CO134
(iv)	16CO135 - 16CO145